

Probability Hardware Report

Chakka Surya Saketh
AI22BTECH11005

Abstract—Use shift registers to create a random number generator for this assignment.

COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K Ω	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE 0: Components used

PROCEDURE

- 1) We connected the 555 timer circuit like the figure 1
- 2) Then, we coupled the 555 timer's clock output to the D-flip flops' clock signal.
- 3) Now we make the circuit for shift registers using a 4 D-Flip flops (using two 7474 IC's)
- 4) Then we connected XOR gate (7486 IC) according to the figure 7
- 5) Then we connected the decoder (7447 IC) and connected its A,B,C,D with Q_0, Q_1, Q_2, Q_3 respectively as per the figure 4
- 6) Make connections between the seven segment display in figure 5 and the 7447 IC in figure 6 as shown in Table
- 7) make connections like Vcc and GND to every IC as per the respective IC pinout for IC's 7474, 7447, 7486.
- 8) Before connecting the power supply, we linked all of the independent components using figure 3.

OUTPUT

Random numbers are generated on the display.

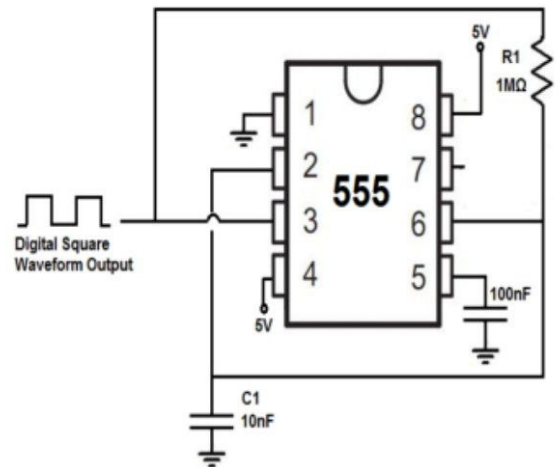


fig:2 Connection in 555 timer circuit

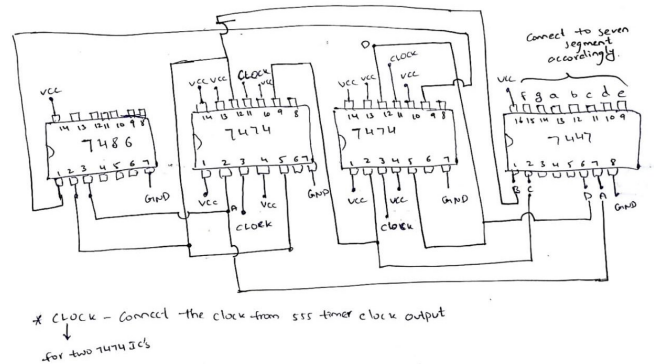


fig:3 circuit connections



fig:4 Connection in Decoder gate

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

fig:5 Connection of seven segmented display with decoder

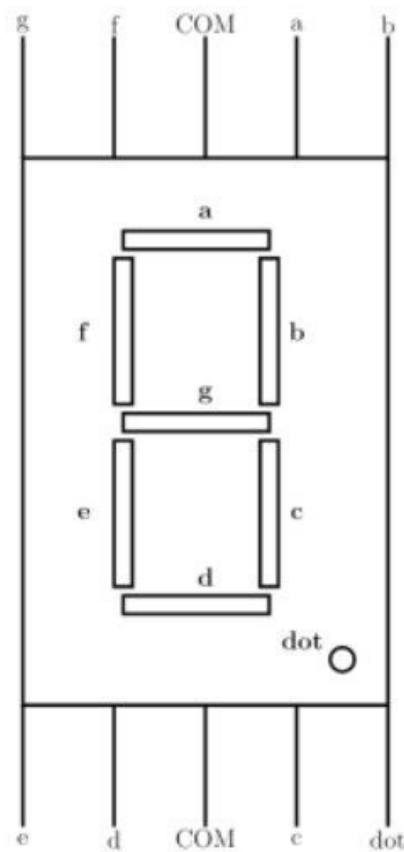


fig:6 Seven segmented display

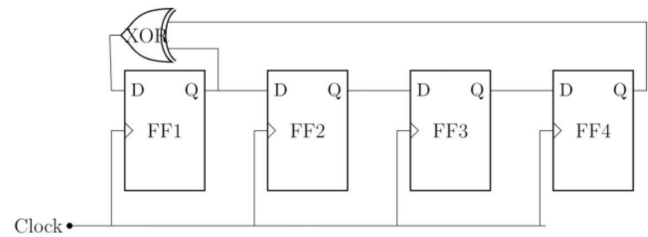


fig:7 Connection in XOR gate

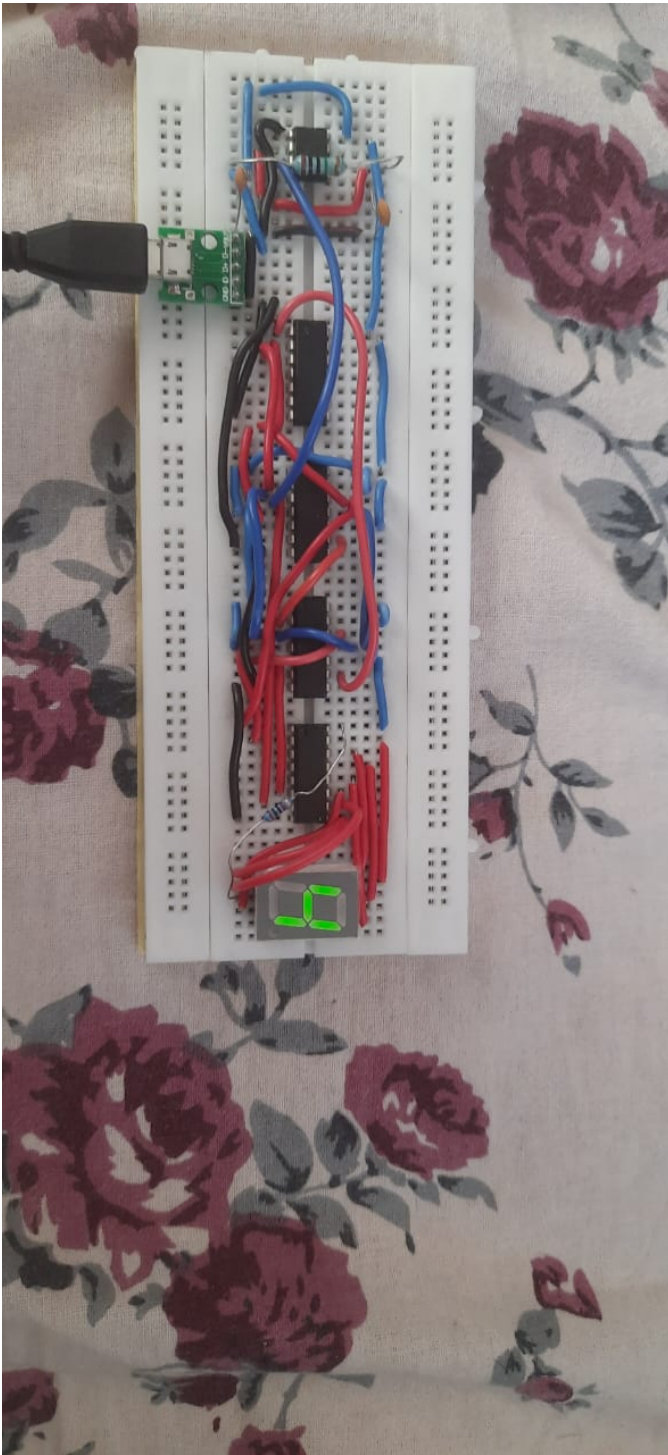


fig:8 output

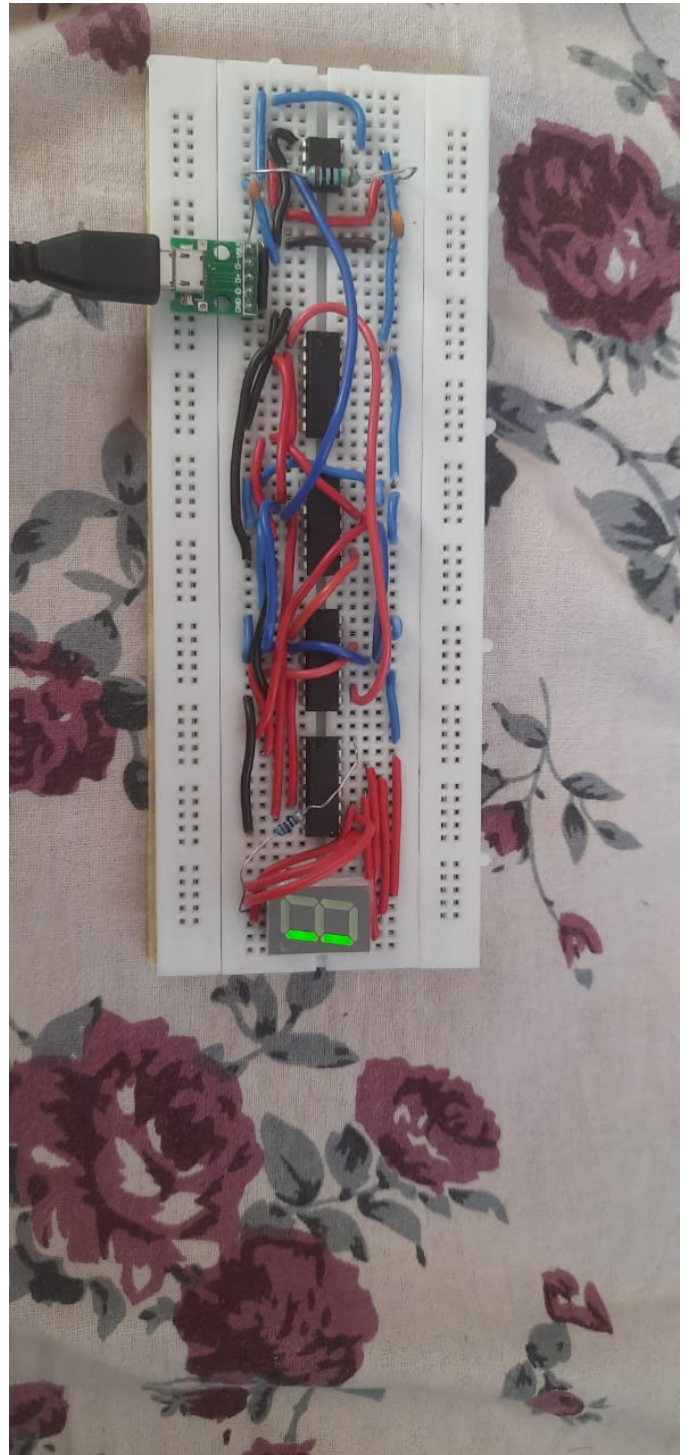


fig:9 output

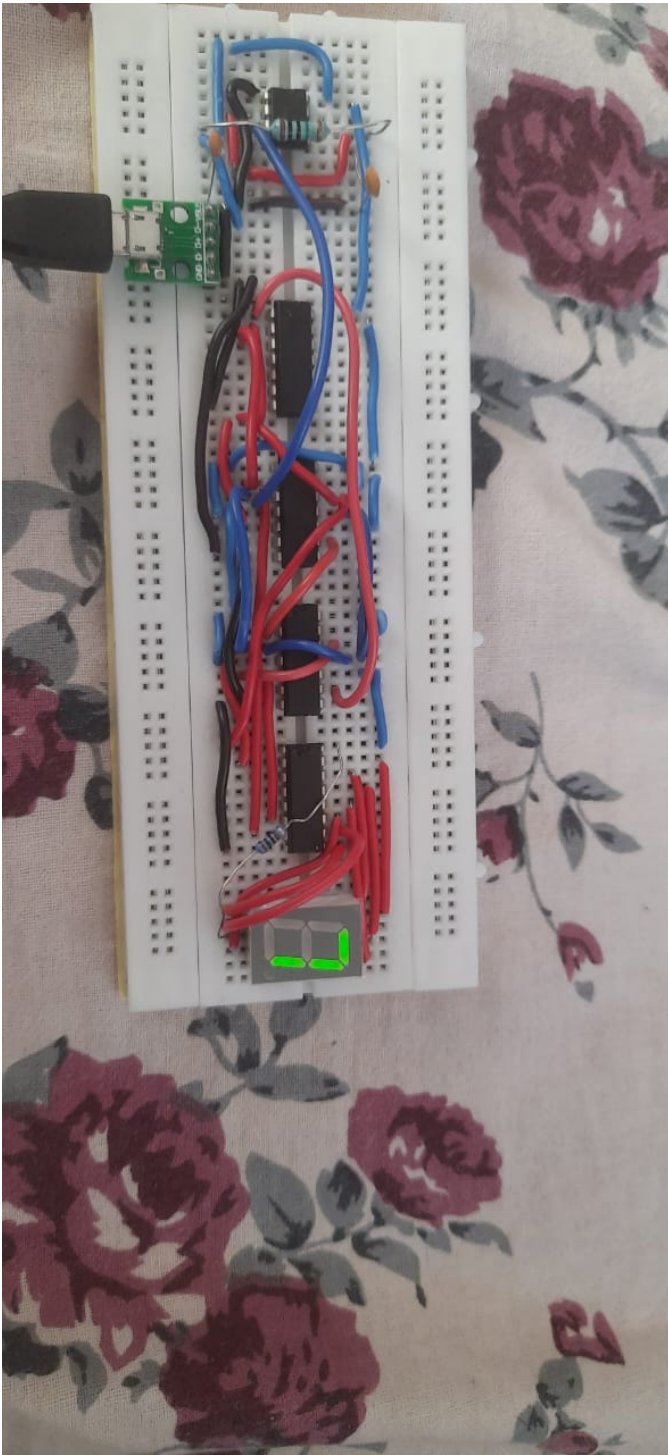


fig:10 output

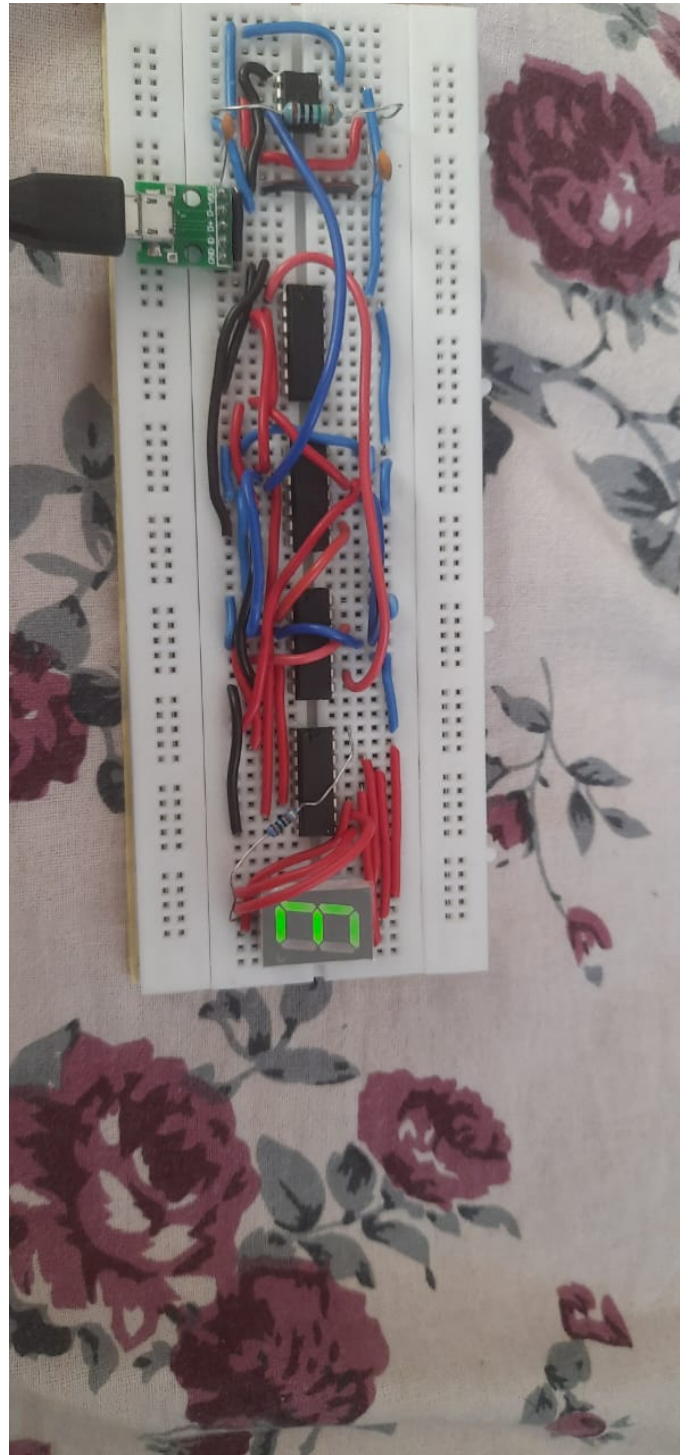


fig:11 output